



UNIVERSITY OF TEHRAN

Electrical and Computer Engineering Department

Digital Logic Design, ECE 367 / Digital Systems I, ECE 894

Spring 1402

Computer Assignment 6

RT Level Component Design and FPGA Implementation - Week 24

Name:

Date:

Username:

1. **RTL Design of a Selection Sorter (ascending order).** A memory block of 256 16-bit words is given that contains binary data. This is an SRAM with a *readMem*, *writeMem*, *rdyMem* and clock control inputs. The memory has a 16-bit *inBus*, a 16-bit *outBus*, and 8 address lines (*addrBus*).
In this assignment you are asked to design a Selection Sorter. The sorter has a *start* signal that begins the sorting of 256 words in the memory block, and a *done* signal that becomes 1 when sorting is complete, and it is waiting for the next start.
 - a. Design an RTL circuit with a datapath and controller for sorting the data in the memory block.
 - b. Write Verilog description of the sorter circuit.
 - c. For initializing the SRAM, create the .hex file according to the attached tutorial and then fill the SRAM with the file.