



**UNIVERSITY OF TEHRAN**  
**Electrical and Computer Engineering Department**  
**Digital Logic Design, ECE 367 / Digital Systems I, ECE 894**  
**Spring 1402**  
**Computer Assignment 4-5**  
**State Machines and Basic RTL**  
**Quartus Pre- and Post-Layout Simulation**


**Name:**

**Date:**

**Username:**

In this assignment, you will design a Multi-channel Synchronous Serial communication Demultiplexer MSSD. The source provides a stream of 1-bit data that includes the size of the data to be transferred, the destination port, and the actual data.

 **Problem Description:** Serial bits of data appear on the *serIn* input of MSSD. Normally, in “no-transmission mode”, *serIn* is 1. Transmission begins when *serIn* makes a 1 to 0 transition. The 0 value bit marks the beginning of the transmission and has no other information. The two bits that follow are the port number, *p*, MSB first in time. The next 4 bits are the number of bytes, *n*, MSB comes first in time. With  $1 + 2 + 4 + n \times 8$  clock cycles after *serIn* becomes 0, it will return to 1 and another transmission begins with another start-bit. Data on *serIn* are synchronized with the MSSD clock, *clk*. This multiplexer extracts the destination code (*d*, two bits) and the number of bytes that will go to the destination port (*n*, 6 bits). Following this, the next  $n \times 8$  bits will be transmitted to port *d*. In addition to the four ports of MSSD, i.e., *p0*, *p1*, *p2*, and *p3*, the active port id, i.e., *d*, an *outValid* signal, and an error signal are the outputs of MSSD. The *outValid* signal remains 1 for as long as actual data is being transmitted to an output port. The error signal should be issued if the value of *serIn* does not become 1 (“no-transmission mode”) after  $1 + 2 + 4 + n \times 8$  clock cycles.



**Simulation:**

- a. Using state machines, counters, shift-registers and other RTL components discussed in class show the design of the MSSD circuit.
- b. In a SystemVerilog module describe individual components of this circuit and wire them together within the MSSD module.
- c. Write a testbench to test your design of MSSD. Perform ModelSim simulation for several destinations and transmit data sizes.

**Netlist Synthesis (basic gates target):**

- a. Take the entire MSSD module into Yosys and synthesize it to our standard library.
- b. Run Verilog simulation to verify the operation of the post-synthesis Yosys output.

**Synthesis and post-synthesis simulation (FPGA target):**

- c. Take the entire MSSD module into Quartus, synthesize it and generate a symbol for it.
- d. Instantiate MSSD within a top-level Quartus Block Diagram, and connect the input output pins.
- e. Synthesize the circuit you generated in Quartus to generate .vo and .sdo files.
- f. Add the post-synthesis output of the previous part to the testbench you generated for simulation part and run the same simulations to compare the results.
- g. Verify timing and operation of the post-synthesis output.

**Deliverables:**

A complete report containing answers to all parts of each question. Your report should include enough design illustration, description, actual data, and output justification. Note that your reports should be well-organized.

---

**Attention:**

Make a *PDF* file of your report and submit it to the course site. Also, compress all files and documents mentioned in the *Deliverables* section into a *zip* file and upload the generated file.